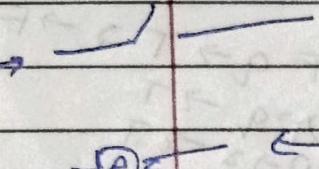


DOOR
play game
Data
and scripts
connected to two
terminals

Applications: Switching Networks: connected to two terminals

open → no current flow
close → current flows

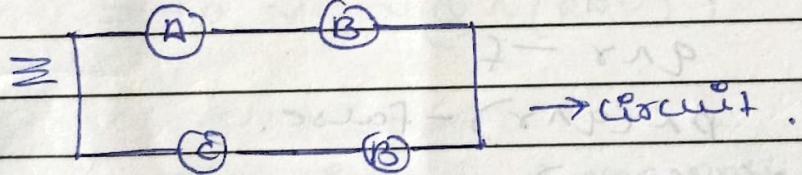

closed switches represent as
open switches represent as

① switches in series $\rightarrow A \cdot B$ or $A \cdot B$


② switches connected in parallel $\rightarrow A + B$ or $A + B$

'1', '0', 'V' \rightarrow logical
'1', '0', '+' \rightarrow in electricals and
(not) (and) (or) circuits

$(A \bar{B}) + (\bar{C}B)$ \rightarrow symbolic representation of circuit




write symbolically: ①

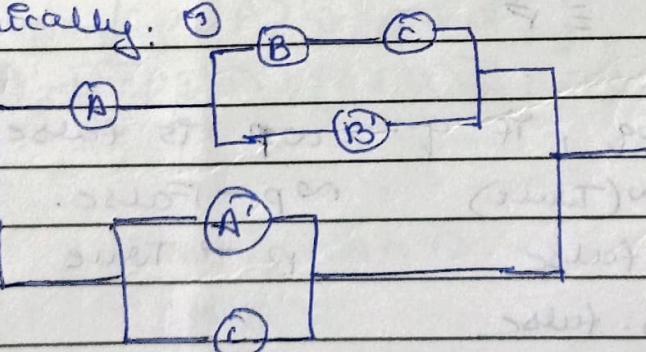

$$\Rightarrow [A \cdot (B \cdot C + B')] + (A' + C) = \{ A \cdot (B \cdot C \vee B') \} + [A' \vee C]$$

(2)

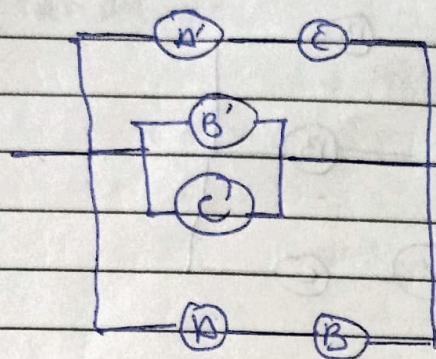

$$\Rightarrow D' \cdot C + (B' + C') + A \cdot B$$

$$\Rightarrow D' \cdot C \vee (B' \vee C') \vee A \cdot B$$


Simplify the above equation.

$$(D' \cdot C) \vee (B' \vee C') \vee (A \cdot B)$$

cannot be simplified.

- (3) Draw a switching network by an equivalent simpler network.


(i)

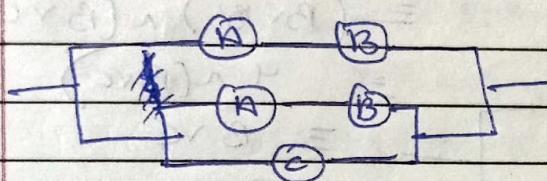


$$(A \wedge B) \vee ((A \wedge B) \cdot C)$$

$$\equiv [(A \wedge B) \vee (A \wedge B)] \vee C$$

$$\equiv (A \wedge B) \vee C$$

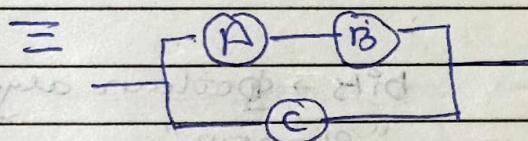

(ii)

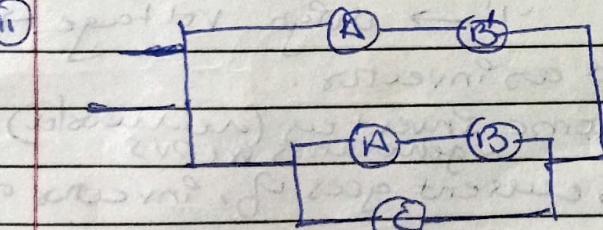

$$(A \wedge B') \vee ((A \wedge B) \vee C)$$


$$\equiv (A \wedge B') \vee (A \wedge B) \vee C$$

$$\equiv A \wedge (B' \vee B) \vee C \quad \because \text{distributive law}$$

$$\equiv (A \wedge T) \vee C \quad \because p' \vee p = t$$

$$\equiv A \vee C$$

Inverse law

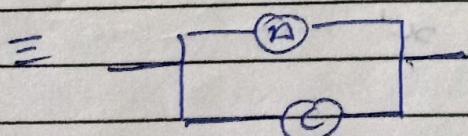


"When same signs
associative law holds
good"

D015

Page No.

Date / /

(ii)

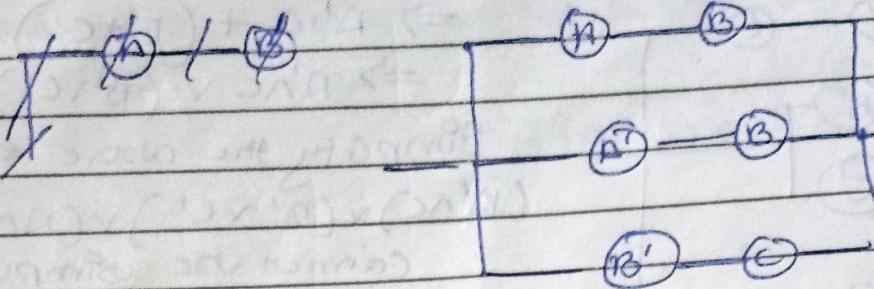

$$(A \wedge B) \vee (A' \wedge B) \vee (B' \wedge C)$$

$$B \wedge (A \vee A') \vee (B' \wedge C) \quad \because \text{Distributive law}$$

$$B \wedge T \vee (B' \wedge C) \quad \because \text{Invert law}$$

$$\cancel{B} = B \vee (B' \wedge C) \quad \because \text{distributive law.}$$


(Absrt)

$$= (B \vee B') \wedge (B \vee C)$$

$$= 1 \wedge (B \vee C)$$

$$= B \vee C$$

$$= B + C$$

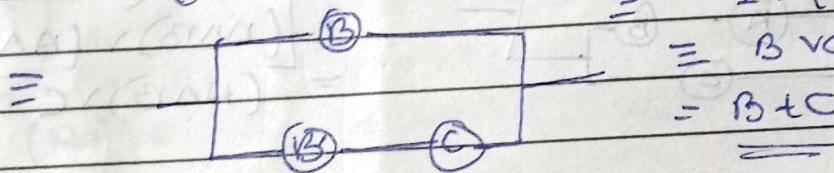

logic "gates":

one or many inputs

but only one output.

bits \rightarrow Boolean algebra

"Shanon"

'0' \rightarrow low voltage \rightarrow false

'1' \rightarrow high voltage \rightarrow true.

① NOT gate: Also called as inverter.


Logic table:

x	x'
0	1
1	0


eg: Home inverters (heat waste)
generators for DVDs

\hookrightarrow current goes off, inverter on &
vice versa

NOT Gate:

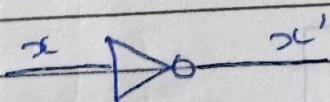



or

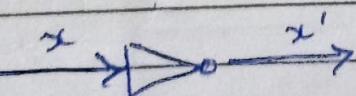

$$x' = \begin{cases} 1 & \text{if } x=0 \\ 0 & \text{if } x=1 \end{cases}$$

② AND gate: x and y are input signals in terms of bits.

$$x \text{ AND } y \equiv xy$$

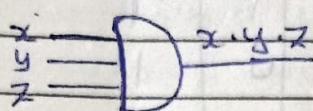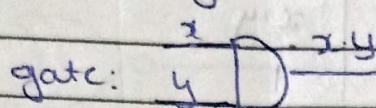

logic table:

x	y	xy
0	0	0
0	1	0
1	0	0
1	1	1

example: examination with internal and external markings.

$$xy = \begin{cases} 1 & \text{if } x=y=1 \\ 0 & \text{otherwise.} \end{cases}$$

③ OR gate: x and y are input signals in terms of bits



$$x+y \equiv X \text{ OR } Y$$

$$x+y = \begin{cases} 1 & \text{if } x=1 \text{ or } y=1 \\ 0 & \text{otherwise.} \end{cases}$$

logic table:


x	y	$x+y$
0	0	0
0	1	1
1	0	1
1	1	1

OR gate:

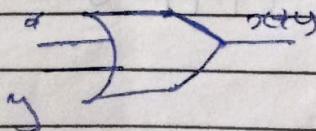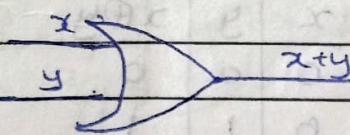

(4)

NAND:

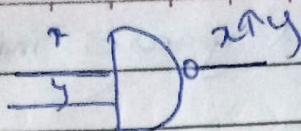


x	y	$\bar{x} \bar{y}$
0	0	1
0	1	1
1	0	1
1	1	0

$$x \otimes y = \begin{cases} 0 & \text{if } x=y=1 \\ 1 & \text{otherwise} \end{cases}$$

(5)

NOR

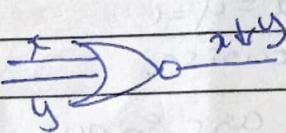


x	y	$\bar{x} \bar{y}$
0	0	1
0	1	0
1	0	0
1	1	0

$$x \oplus y = \begin{cases} 0 & \text{if } x=y=0 \\ 1 & \text{otherwise} \end{cases}$$

(6)

XOR : $x \oplus y$

xor is same why

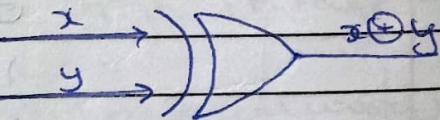


x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

$$x \oplus y = \begin{cases} 0 & \text{x and y same value} \\ 1 & \text{otherwise} \end{cases}$$

⑦ XNOR : Exclusive NOR Gate. \equiv Biconditional


$x \text{ XNOR } y$

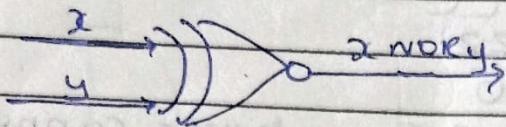

x	y	$x \text{ XNOR } y$
0	0	1
0	1	0
1	0	0
1	1	1


Circuits with logic gates \rightarrow Combinational Circuit
circuits with switches and wires \rightarrow switching circuits

Combinational Circuit:

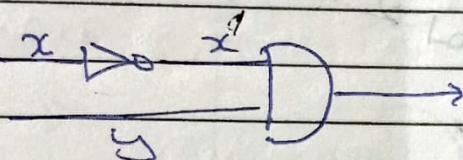

xyz — Boolean expression.

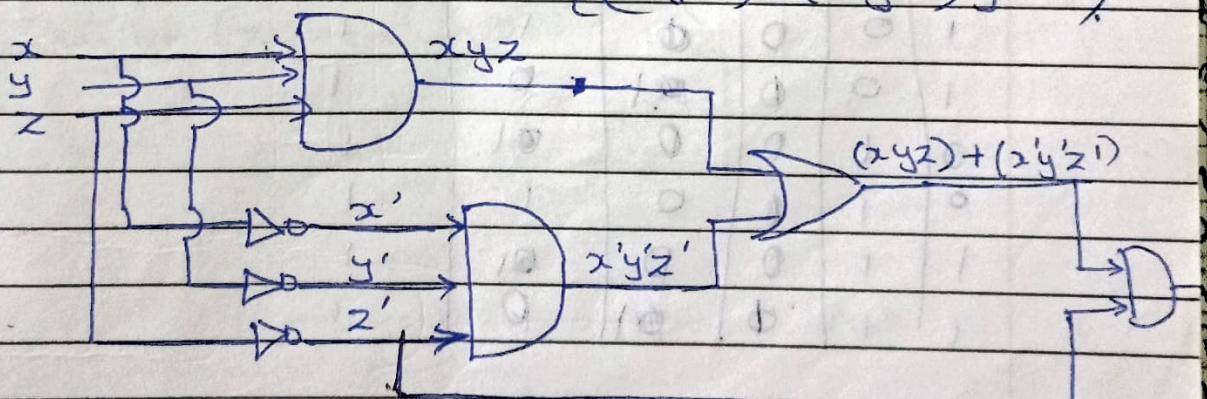① $[(xyz) + (x'y'z)](xyz)$ (Actual question)
 $\quad\quad\quad [(xyz) + (x'y'z)]z'$)




If possible write the simpler combinational circuit which is equivalent to given boolean expression.

Boolean function,

$$\begin{aligned}
 f(xyz) &= [(xyz) + (x'y'z)]z' \\
 &= [z(xy + x'y')]z' \\
 &= zz' \\
 &= 0
 \end{aligned}$$

* got contradiction hence cannot simplify
and go ahead with the circuit.

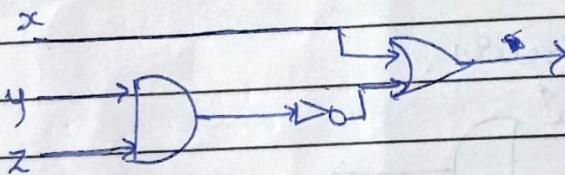
Find the output of the combinational circuit,
also construct a logic table.



$$x + (y'z')'$$

y	x	z	yz	$(yz)'$	$x + (yz)'$
0	0	0	0	1	1
0	0	1	0	1	1
1	0	0	0	1	1
1	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	1	1
1	1	0	0	0	1
1	1	1	1	0	1

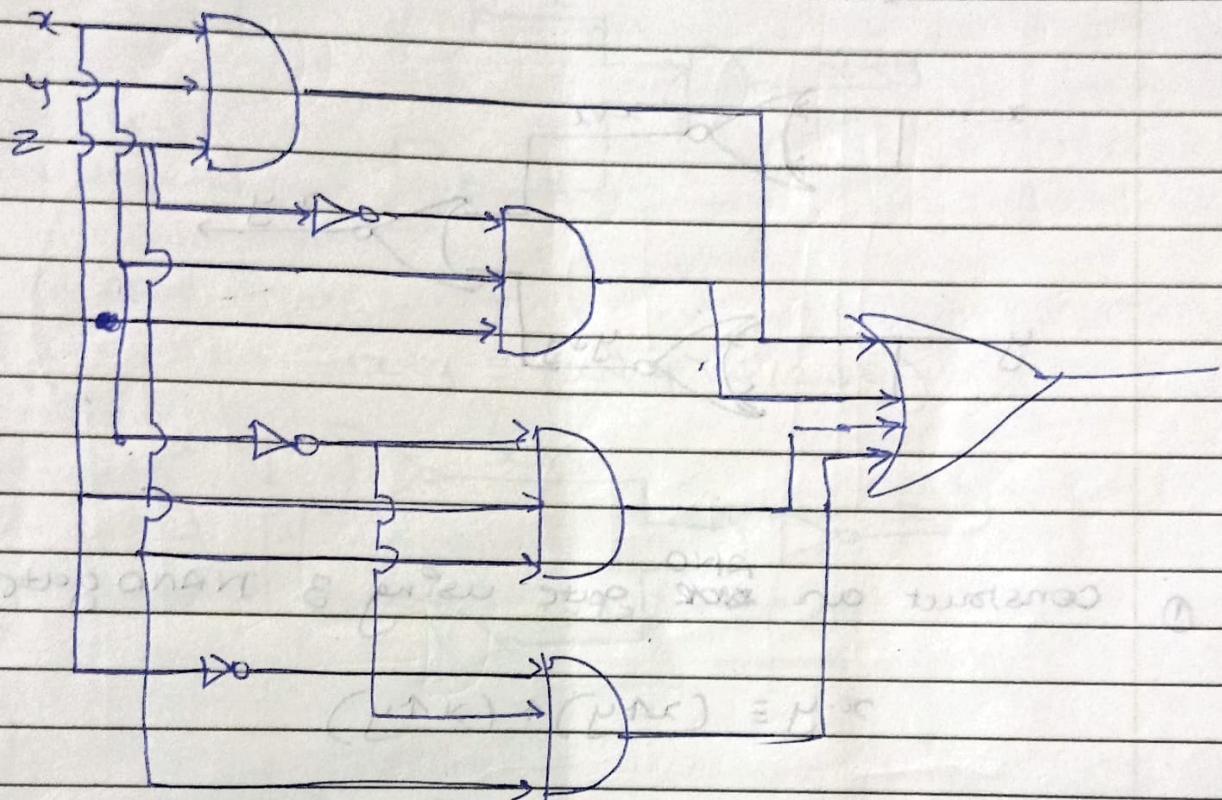Find the output produced by the combinational circuit also find the simple CS equivalent to it




$$\begin{aligned}
 f(xyz) &= (xyz) + (xyz') + (xy'z) + (x'y'z) = xy + y'z \\
 &= xy(z+z') + (xy'+x'y)z = (y'z)(x+x') \\
 &= xy + (xy' + x'y)z = y'z
 \end{aligned}$$

Construct an AND gate using 3 NOR gates.


$$x \cdot y \equiv (x \downarrow x) \downarrow (y \downarrow y)$$

$$xy = \overline{x+y}$$

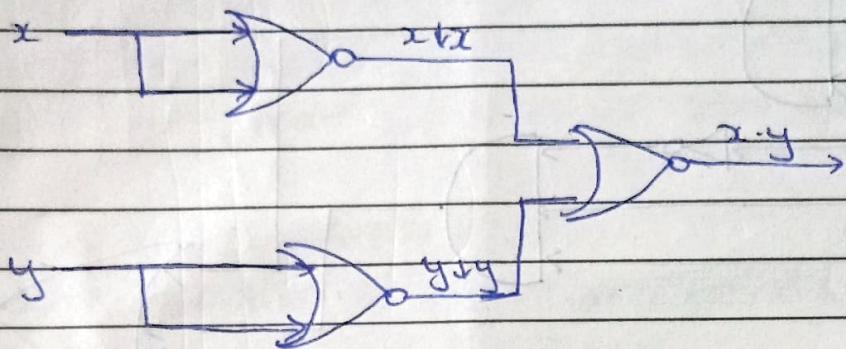


- ① Construct an ~~NOR~~^{AND} gate using 3 NANO gate
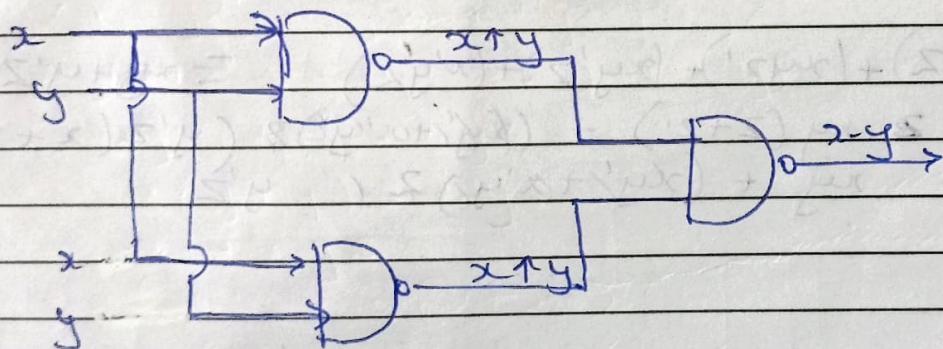
$$x \cdot y \equiv (x \uparrow y) \uparrow (x \uparrow y)$$




- ② Implement by only 2 NANO gates

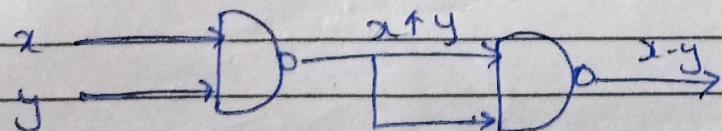


Construct OR gate using 3 NAND gate

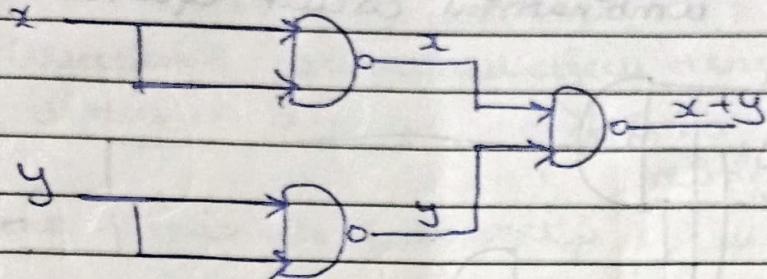
$$x+y = (\bar{x} \cdot x) \uparrow (\bar{y} \cdot y)$$


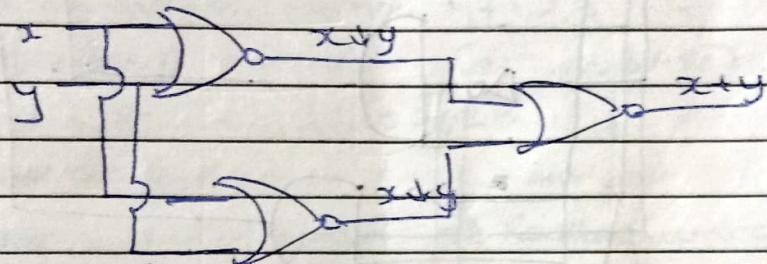
$$x+y = (\bar{x} \cdot y) \downarrow (\bar{x} \cdot y)$$




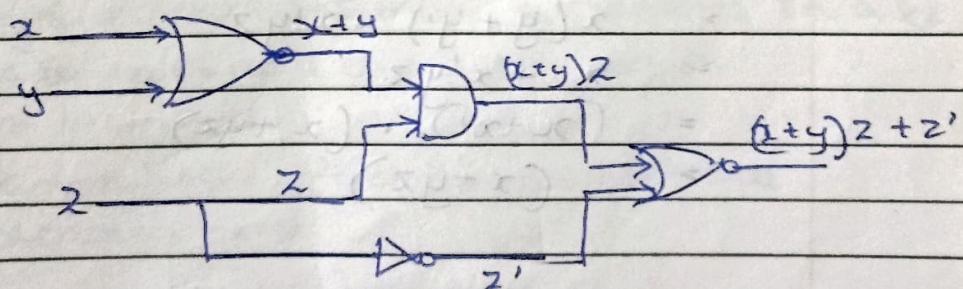make a combinational circuit that yields the boolean expression $(x+y)z + z'$ as its output.




Construct a combinational circuit for the Boolean expression $xyz + xyz' + xy'z + x'y'z + xy'z'$. Find a simplified combinational circuit equivalent to it.

Soln:

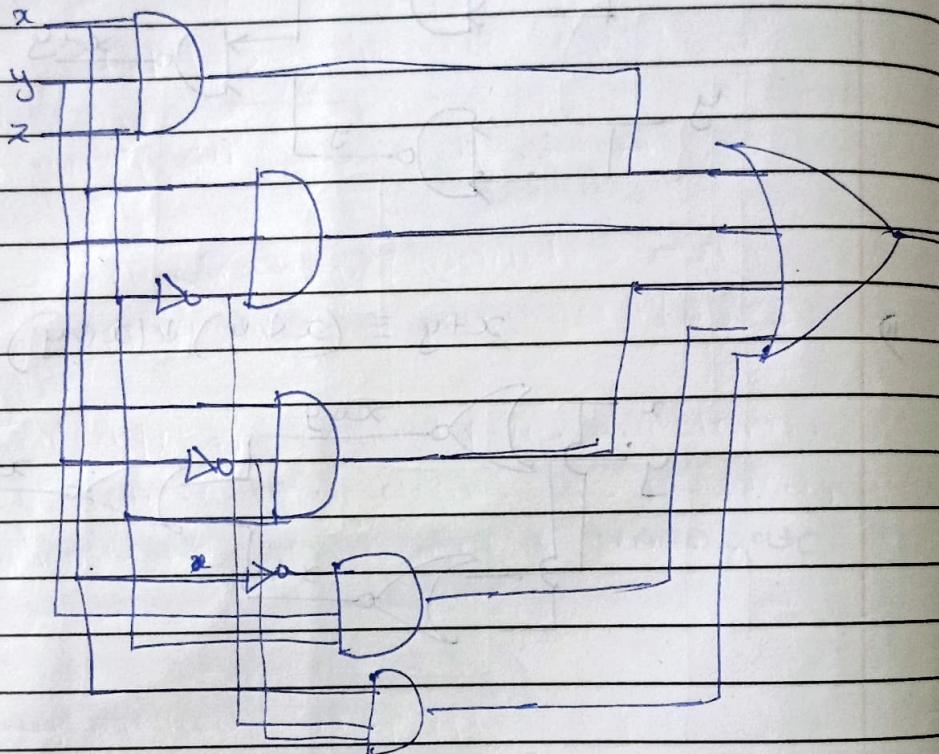
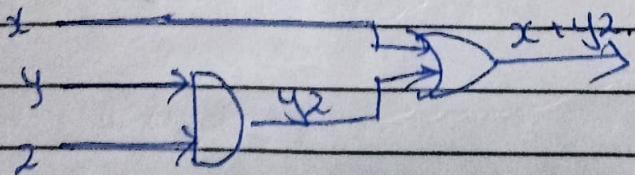
$$\begin{aligned}
 f(x,y,z) &= xyz + xyz' + xy'z + x'y'z + xy'z' \\
 &= xy(z+z') + xy'(z+z') + x'y'z \\
 &= xy + xy' + x'y'z \\
 &= x(y+y') + x'y'z \\
 &= x + x'y'z \\
 &= (x+x') \cdot (x+y'z) \\
 &= (x+y'z)
 \end{aligned}$$



∴ equivalent combinational circuit is